

# Numbers in the Fibonacci Sequence Circuit

## PC/CP220 Project Phase I

Nicholas Sam  
190148430  
Fall 2020

### Description

The Fibonacci sequence is a sequence of numbers that appeared in historical mathematics. It is described as a sequence that starts with the numbers 0 and 1, where each continuing number is the sum of the two previous numbers. The equation to find a number of the sequence can be denoted as:

$$F_n = F_{n-1} + F_{n-2}, \text{ where } F_0 = 0, F_1 = 1$$

### Inputs

The Numbers in the Fibonacci Sequence Circuit will have three inputs,  $a_0$  to  $a_2$ , which gives binary representation to the  $n$ th number of the sequence. ( $a_0$  is the least significant bit)

### Outputs

The Numbers in the Fibonacci Sequence Circuit will have four outputs,  $b_0$  to  $b_3$ , which gives binary representation to the value of the  $n$ th number of the sequence. For example, the binary input of 3 (011) will output the 3rd number of the sequence, which is 2 (010).

### Notes

Some sources will display that the Fibonacci sequence starts at the values 1 and 1, rather than 0 and 1. For the purposes of this project, the 0th number of the sequence will be 0, and the 1st will be 1.