

# Numbers in the Fibonacci Sequence Circuit

## PC/CP220 Project Phase II

Nicholas Sam

190148430

Fall 2020

### Equations

Truth table of the Numbers in the Fibonacci Sequence Circuit

Number ( $n$ )	$a_2a_1a_0$	$n^{th}$ term in the Fibonacci Sequence	$b_3b_2b_1b_0$
0	000	0	0000
1	001	1	0001
2	010	1	0001
3	011	2	0010
4	100	3	0011
5	101	5	0101
6	110	8	1000
7	111	13	1101

Truth tables for each bit

$a_2$	$a_1$	$a_0$	$b_3$	$b_2$	$b_1$	$b_0$
0	0	0	0	0	0	0
0	0	1	0	0	0	1
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	0	1	1
1	0	1	0	1	0	1
1	1	0	1	0	0	0
1	1	1	1	1	0	1

A K-Map can be used to determine the simplest equation for each bit.

$b_3$

$b_3$		$a_0$	
		0	1
$a_2a_1$	00	0	0
	01	0	0
	11	1	1
	10	0	0

- $a_2a_1$  ( $a_0$  is irrelevant)

$$b_3 = a_2a_1$$

$b_2$

$b_2$		$a_0$	
		0	1
$a_2a_1$	00	0	0
	01	0	0
	11	0	1
	10	0	1

- $a_2a_0$  ( $a_1$  is irrelevant)

$$b_2 = a_2a_0$$

$b_1$

$b_1$		$a_0$	
		0	1
$a_2a_1$	00	0	0
	01	0	1
	11	0	0
	10	1	0

- $\bar{a}_2a_1a_0$

- $a_2\bar{a}_1\bar{a}_0$

$$b_2 = \bar{a}_2a_1a_0 + a_2\bar{a}_1\bar{a}_0$$

$b_0$

$b_0$		$a_0$	
		0	1
$a_2 a_1$	00	0	1
	01	1	0
	11	0	1
	10	1	1

- $\bar{a}_1 a_0$  ( $a_2$  is irrelevant)
- $a_2 \bar{a}_1$  ( $a_0$  is irrelevant)
- $\bar{a}_1 a_0$  ( $a_2$  is irrelevant)
- $\bar{a}_2 a_1 \bar{a}_0$

$$b_0 = \bar{a}_1 a_0 + a_2 \bar{a}_1 + \bar{a}_1 a_0 + \bar{a}_2 a_1 \bar{a}_0$$

Testing

$b_3$

```
(%i1) b3:a2 and a1;
(%o1)      a2^a1

(%i2) b3,a2=false,a1=false,a0=false;
(%o2)      false

(%i3) b3,a2=false,a1=false,a0=true;
(%o3)      false

(%i4) b3,a2=false,a1=true,a0=false;
(%o4)      false

(%i5) b3,a2=false,a1=true,a0=true;
(%o5)      false

(%i6) b3,a2=true,a1=false,a0=false;
(%o6)      false

(%i7) b3,a2=true,a1=false,a0=true;
(%o7)      false

(%i8) b3,a2=true,a1=true,a0=false;
(%o8)      true

(%i9) b3,a2=true,a1=true,a0=true;
(%o9)      true
```

Matches the original truth table, therefore the equation is correct.

$b_2$

```
(%i1) b2:a2 and a0;  
(%o1)  a2^a0  
  
(%i2) b2,a2=false,a1=false,a0=false;  
(%o2)  false  
  
(%i3) b2,a2=false,a1=false,a0=true;  
(%o3)  false  
  
(%i4) b2,a2=false,a1=true,a0=false;  
(%o4)  false  
  
(%i5) b2,a2=false,a1=true,a0=true;  
(%o5)  false  
  
(%i6) b2,a2=true,a1=false,a0=false;  
(%o6)  false  
  
(%i7) b2,a2=true,a1=false,a0=true;  
(%o7)  true  
  
(%i8) b2,a2=true,a1=true,a0=false;  
(%o8)  false  
  
(%i9) b2,a2=true,a1=true,a0=true;  
(%o9)  true
```

Matches the original truth table, therefore the equation is correct.

$b_1$

```
(%i1) b1:((not a2) and a1 and a0) or (a2 and (not a1) and (not a0));  
(%o1)  ¬a2^a1^a0∨a2^¬a1^¬a0
```

```
(%i2) b1,a2=false,a1=false,a0=false;  
(%o2)  false
```

```
(%i3) b1,a2=false,a1=false,a0=true;  
(%o3)  false
```

```
(%i4) b1,a2=false,a1=true,a0=false;  
(%o4)  false
```

```
(%i5) b1,a2=false,a1=true,a0=true;  
(%o5)  true
```

```
(%i6) b1,a2=true,a1=false,a0=false;  
(%o6)  true
```

```
(%i7) b1,a2=true,a1=false,a0=true;  
(%o7)  false
```

```
(%i8) b1,a2=true,a1=true,a0=false;  
(%o8)  false
```

```
(%i9) b1,a2=true,a1=true,a0=true;  
(%o9)  false
```

Matches the original truth table, therefore the equation is correct.

$b_0$

```
(%i1) b0:((not a2) and a1 and (not a0)) or (a2 and (not a1)) or ((not a1) and a0) or (a2 and a0);
(%o1)  -a2^a1^~a0^a2^~a1^~a1^a0^a2^a0

(%i2) b0,a2=false,a1=false,a0=false;
(%o2)  false

(%i3) b0,a2=false,a1=false,a0=true;
(%o3)  true

(%i4) b0,a2=false,a1=true,a0=false;
(%o4)  true

(%i5) b0,a2=false,a1=true,a0=true;
(%o5)  false

(%i6) b0,a2=true,a1=false,a0=false;
(%o6)  true

(%i7) b0,a2=true,a1=false,a0=true;
(%o7)  true

(%i8) b0,a2=true,a1=true,a0=false;
(%o8)  false

(%i9) b0,a2=true,a1=true,a0=true;
(%o9)  true
```

Matches the original truth table, therefore the equation is correct.

## Summary

The equations of the output bits are:

- $b_3 = a_2 a_1$
- $b_2 = a_2 a_0$
- $b_1 = \bar{a}_2 a_1 a_0 + a_2 \bar{a}_1 \bar{a}_0$
- $b_0 = \bar{a}_2 a_1 \bar{a}_0 + a_2 \bar{a}_1 + \bar{a}_1 a_0 + a_2 a_0$

The equations were tested in Maxima, and were proven to be correct.